

Title: R-S FLIP FLOPS**Materials:**

- [1] 7400 2-input NAND gate IC
- [1] clock (single pulses)

Procedure:

1. On a separate sheet of paper, **draw** a logic diagram for the R-S flip-flop shown in Fig. 9(a). Use two 2-input NAND gates.
2. Insert the 7400 into the breadboard.
3. Construct the circuit you drew in step 1.
4. Operate the input switches as shown in Table 9-1. Observe and record the results in the output columns. **Get Instructor's Signature.**
5. **Have Instructor check your pulse clock if you're not sure that it works.**
6. In the rightmost column of Table 9-1 write the name of the condition of the outputs. Use term "hold", "set", or "reset".
7. On a separate sheet of paper, **draw** a logic diagram for the clocked R-S flip flop shown in Fig. 9(b). Use four 2-input NAND gates.
8. Construct the circuit you drew in step 6.
9. Operate the input switches as shown in Table 9-2 and record the output results. **Get Instructor's Signature.**

Questions: (answer on a separate piece of paper – **"Draw"** means you must use a template):

1. Describe the input conditions on the *R-S flip-flop* for the set, reset, and hold conditions. Label the inputs R & S and the outputs Q and \bar{Q} .
2. Describe the input conditions on the *clocked R-S flip-flop* for the set, reset, and hold conditions. Label the inputs R & S and the outputs Q and \bar{Q} .
3. Describe the input conditions on the *R-S flip-flop* that are considered the prohibited state/condition.
4. Describe the input conditions on the *clocked R-S flip-flop* that are considered the prohibited state/condition.

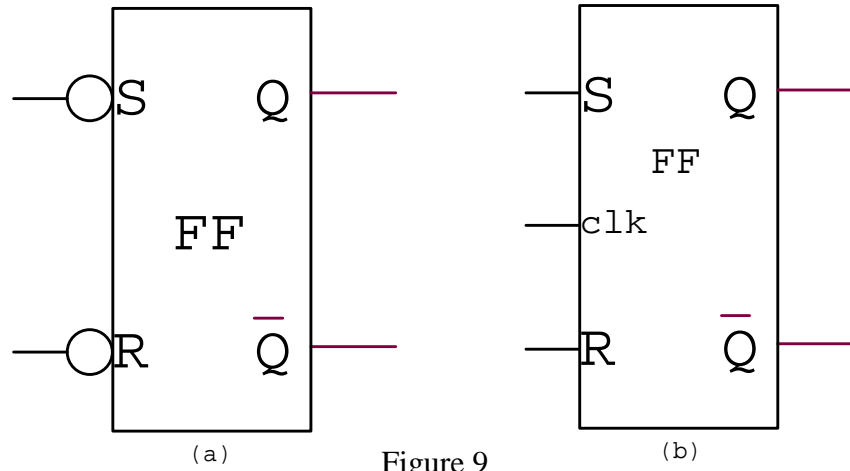


Figure 9

Inputs		Outputs		
S	R	Q	\bar{Q}	Name of Condition
0	0			Prohibited
0	1			
1	0			
1	1			
		hold, set, or reset		

Table 9-1 R-S Flip-Flop

Inputs			Outputs				
Clock	Data		Before clock pulse		After clock pulse		Name of Condition
	S	R	Q	\bar{Q}	Q	\bar{Q}	
↑	0	0	0	1			
↑	0	1	0	1			
↑	1	0	0	1			
↑	1	1	0	1			Prohibited
↑	0	0	1	0			
↑	0	1	1	0			
↑	1	0	1	0			
↑	1	1	1	0			Prohibited
							hold, reset, or set

Table 9-2 Clocked R-S Flip-Flop